
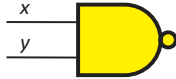
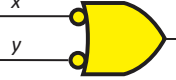
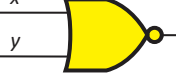
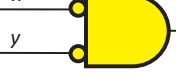
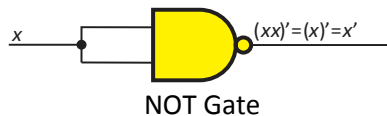
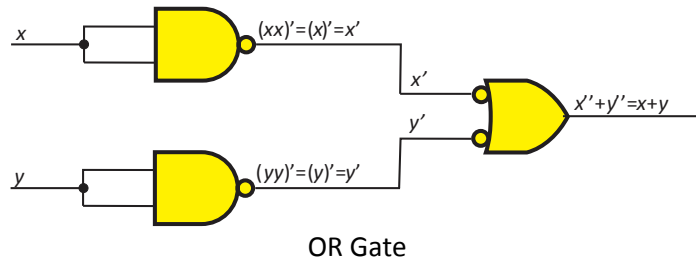
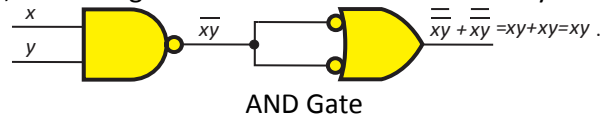
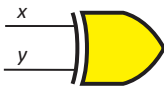


Name	Graphic Symbol	Algebraic Function	Truth Table
NAND		$F(x,y) = (xy)' = \overline{xy}$ $F = \overline{xy}$	$x \quad y \quad F$
			0 0 1
			0 1 1
			1 0 1
			1 1 0
NAND		$F(x,y) = x' + y' = \overline{x+y}$ $F = \overline{x+y}$	$\overline{x} \quad \overline{y} \quad F$
			1 1 1
			1 0 1
			0 1 1
			0 0 0
NOR		$F(x,y) = (x+y)' = \overline{x+y}$ $F = \overline{x+y}$	$x \quad y \quad F$
			0 0 1
			0 1 0
			1 0 0
			1 1 0
NOR		$F(x,y) = x' \cdot y' = \overline{x+y}$ $F = \overline{x+y}$	$\overline{x} \quad \overline{y} \quad F$
			1 1 1
			1 0 0
			0 1 0
			0 0 0

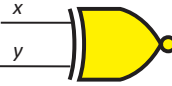We know that all logic functions can be constructed from AND, OR, and NOT gates. The foregoing statement is equivalent to saying that the collection of gates including AND, OR, and NOT is functionally complete. To demonstrate that a NAND gate is functionally complete, we need to show that the AND, OR, and NOT gates can be constructed from only NAND gates.



Name	Graphic Symbol	Algebraic Function	Truth Table		
XOR (Exclusive-OR)		$F = x \oplus y$	x	y	F
			0	0	0
			0	1	1
			1	0	1
			1	1	0
Exclusive-NOR		$F = \overline{x \oplus y}$	x	y	F
			0	0	1
			0	1	0
			1	0	0
			1	1	1

In-class exercise: Using only NAND gates draw the logic diagram for the Boolean function $F(x, y, z) = xy + y'z$.

