

Figure 3.6 A Three-Input OR Gate Representing  $x + y + z$

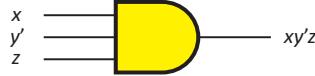


Figure 3.7 A Three-Input AND Gate Representing  $xy'z$


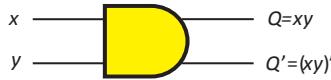


Figure 3.8 AND Gate with Two Inputs and Two Outputs

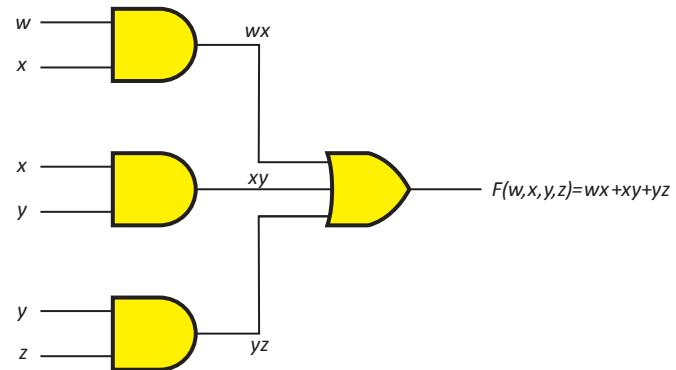In-class Exercise: Draw the logic diagram for the Boolean function  $F(w, x, y, z) = wx + xy + yz$ .



$$F(w, x, y, z) = wx + xy + yz$$