

Logic circuits

- combinational logic (no memory)
- sequential logic (memory)