

- Half-adder
- Full-adder
- Ripple-carry adder
- Decoder
- Multiplexer
- Parity Checker
- 4-Bit Shifter
- 2-Bit ALU
- 2-Bit Multiplier