

1. Feedback
2. Cross-coupled NOR Gates
3. Cross-coupled NAND Gates
4. Clocks and Flip-Flops
5. Ad-hoc design of a SR Flip-Flop
6. Characteristic Table
7. Truth Table
8. Excitation Table

- Memory is implemented by employing feedback.

 


FIGURE 3.29 Example of Simple Feedback


 



FIGURE 3.31 (a) Binary Cell implemented using cross coupled NOR gates

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 0          | 0            | 0             | 0          |
| 0          | 0            | 1             | 1          |
| 0          | 1            | 0             | 0          |
| 0          | 1            | 1             | 0          |
| 1          | 0            | 0             | 1          |
| 1          | 0            | 1             | 1          |
| 1          | 1            | 0             | undefined  |
| 1          | 1            | 1             | undefined  |


Table 3.31 (a) Cross-coupled NOR gate Binary Cell  
Characteristic Table

 


| Inputs |       | Present State | Next State |
|--------|-------|---------------|------------|
| SET    | RESET | $Q(t)$        | $Q(t+1)$   |
| 0      | 0     | 0             | 0          |

 


| Inputs |       | Present State | Next State |
|--------|-------|---------------|------------|
| SET    | RESET | $Q(t)$        | $Q(t+1)$   |
| 0      | 0     | 1             | 1          |

 


| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 0          | 1            | 0             | 0          |

 

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 0          | 1            | 1             | 0          |

 


| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 1          | 0            | 0             | 1          |

 

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 1          | 0            | 1             | 1          |

 - Binary Cell Characteristics (implemented using cross-coupled NAND gates)
  - o When  $SET = RESET = 1$ , the Binary Cell retains its original state.
  - o When  $SET = 0$  and  $RESET = 1$ ,  $Q = 1$  – the Binary Cell is set.
  - o When  $SET = 1$  and  $RESET = 0$ ,  $Q = 0$  – the Binary Cell is reset.
  - o When  $SET = 0$  and  $RESET = 0$ ,  $Q = ?$  – Invalid control: Don't do.



Binary Cell implemented using cross coupled NAND gates

| Inputs |       | Present State | Next State |
|--------|-------|---------------|------------|
| SET    | RESET | $Q(t)$        | $Q(t + 1)$ |
| 0      | 0     | 0             | undefined  |
| 0      | 0     | 1             | undefined  |
| 0      | 1     | 0             | 1          |
| 0      | 1     | 1             | 1          |
| 1      | 0     | 0             | 0          |
| 1      | 0     | 1             | 0          |
| 1      | 1     | 0             | 0          |
| 1      | 1     | 1             | 1          |

Table 3.32 (a) Cross-coupled NAND gate Binary Cell  
Characteristic Table

 


Figure 3.32 (a-1) Binary Cell implemented using cross coupled NAND gates

| Inputs |       | Present State | Next State |
|--------|-------|---------------|------------|
| SET    | RESET | $Q(t)$        | $Q(t + 1)$ |
| 0      | 1     | 0             | 1          |

 


Figure 3.32 (a-2) Binary Cell implemented using cross coupled NAND gates

| Inputs |         | Present State | Next State |
|--------|---------|---------------|------------|
| $SET$  | $RESET$ | $Q(t)$        | $Q(t+1)$   |
| 0      | 1       | 1             | 1          |

 


Figure 3.32 (a-3) Binary Cell implemented using cross coupled NAND gates

| Inputs |         | Present State | Next State |
|--------|---------|---------------|------------|
| $SET$  | $RESET$ | $Q(t)$        | $Q(t+1)$   |
| 1      | 0       | 0             | 0          |

 


Figure 3.32 (a-4) Binary Cell implemented using cross coupled NAND gates

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 1          | 0            | 1             | 0          |

 


Figure 3.32 (a-5) Binary Cell implemented using cross coupled NAND gates

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 1          | 1            | 0             | 0          |

 


Figure 3.32 (a-6) Binary Cell implemented using cross coupled NAND gates

| Inputs     |              | Present State | Next State |
|------------|--------------|---------------|------------|
| <i>SET</i> | <i>RESET</i> | $Q(t)$        | $Q(t + 1)$ |
| 1          | 1            | 1             | 1          |