

Recall the Present-State-Next-State Table constructed in Step 2.

Present State		Input		Next State		Output	
A	B	X		A	B	Z	
0	0	0		0	0	0	0
	0	1		1	0	1	0
1	0	0		3	1	1	1
	0	1		2	1	0	0
2	1	0		0	0	0	1
	1	0		1	0	1	0
3	1	1		2	1	0	1
	1	1		0	0	0	1

Present-State-Next-State Table


Add input control signals for D and JK Flip-Flops.

Present State		Input		Next State		Output			D_A	D_B		J_A	K_A	J_B	K_B
A	B	X		A	B	Z									
0	0	0		0	0	0	0		0	0		0	x	0	x
	0	1		1	0	1	0		0	1		0	x	1	x
1	0	0		3	1	1	1		1	1		1	x	x	0
	0	1		2	1	0	0		1	0		1	x	x	1
2	1	0		0	0	0	1		0	0		x	1	0	x
	1	0		1	0	1	0		0	1		x	1	1	x
3	1	1		2	1	0	1		1	0		x	0	x	1
	1	1		0	0	0	1		0	0		x	1	x	1

Next-State Decoder


$Q(t)$	$\rightarrow Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

JK Excitation Table

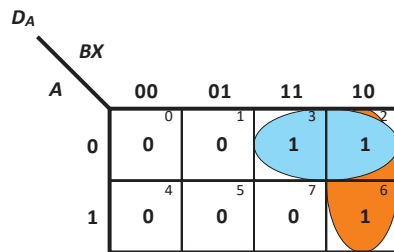


$$D_A = \overline{A}B + BX$$

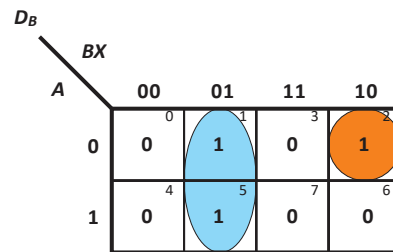
Count the cost: 5 2-input gates; 1 3-input gate



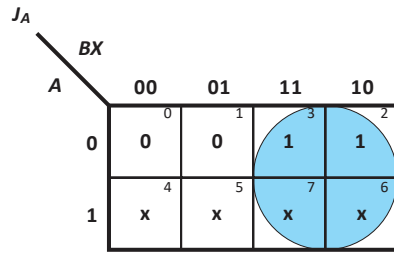
$$D_B = \overline{B}X + \overline{A}B\overline{X}$$




$$J_A = B$$

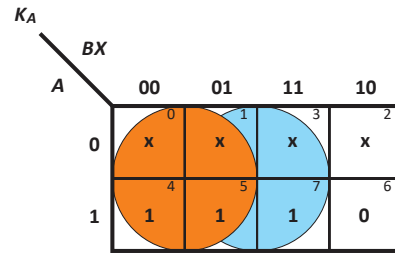

$$K_A = \overline{B} + X$$

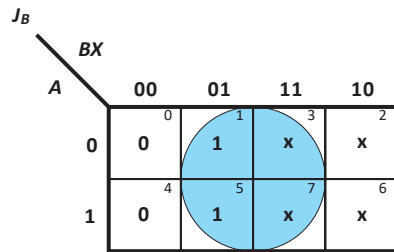

$$J_B = X$$

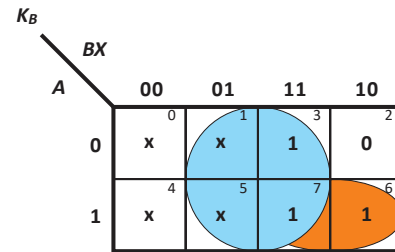

$$K_B = X + AB$$

Count the cost: 3 2-input gates
Choose the JK Flip-Flop implementation