

A sequential circuit has one flip-flop, two inputs, X and Y , and one output D . It consists of a full-subtractor circuit connected to a JK flip-flop, as shown. Fill in the truth table for this sequential circuit by completing the Next State and Output columns.


| Inputs | | | Outputs | |
|--------|-----|----------|---------|-----------|
| X | Y | B_{in} | D | B_{out} |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Truth table for full-subtractor

X : Minuend, Y : Subtrahend, D : Difference, B_{in} : Borrow-in, B_{out} : Borrow-out

| Present State $Q(t)$ | Inputs | | Next State $Q(t + 1)$ | Output D |
|-------------------------|--------|-----|--------------------------|---------------|
| | X | Y | | |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

Next State Table to Complete

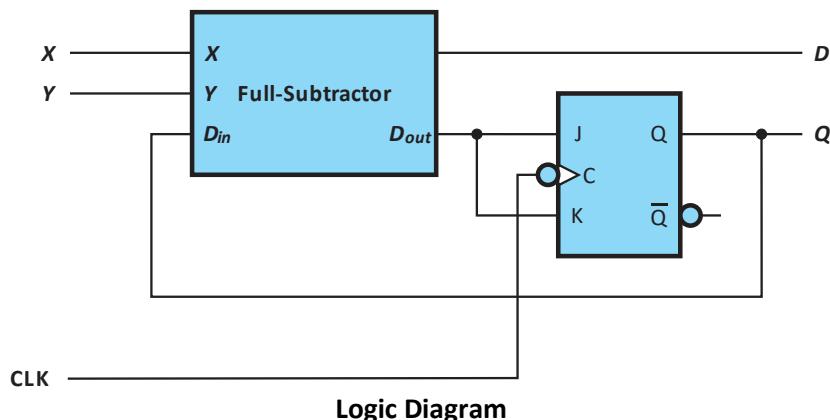

| Present State $Q(t)$ | Inputs X | Inputs Y | Next State $Q(t + 1)$ | Output D |
|-------------------------|---------------|---------------|--------------------------|---------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Next State Table

Solution

$$B_{in} = Q(t), B_{out} = D$$

| X | Y | Inputs | | Outputs | |
|---|---|----------|---|-----------|---|
| | | B_{in} | D | B_{out} | D |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 |