

Term	Discussion
Control Word	A set of signals that executes a microoperation.
Microoperation	A register transfer or other operation that the CPU can execute in a single clock cycle.
Hardwired Control	Directly connects the control lines to the actual machine instructions.
Microprogrammed Control	Employs software consisting of microinstructions that carry out an instruction's microoperations.

4.13.2 Hardwired Control

Bus Address	Component
0	Memory
1	MAR
2	PC
3	MBR
4	AC
5	InReg
6	OutReg
7	IR

Destination				Origin		
IR			to	MAR		
7				1		
P ₅	P ₄	P ₃		P ₂	P ₁	P ₀
1	1	1		0	0	1

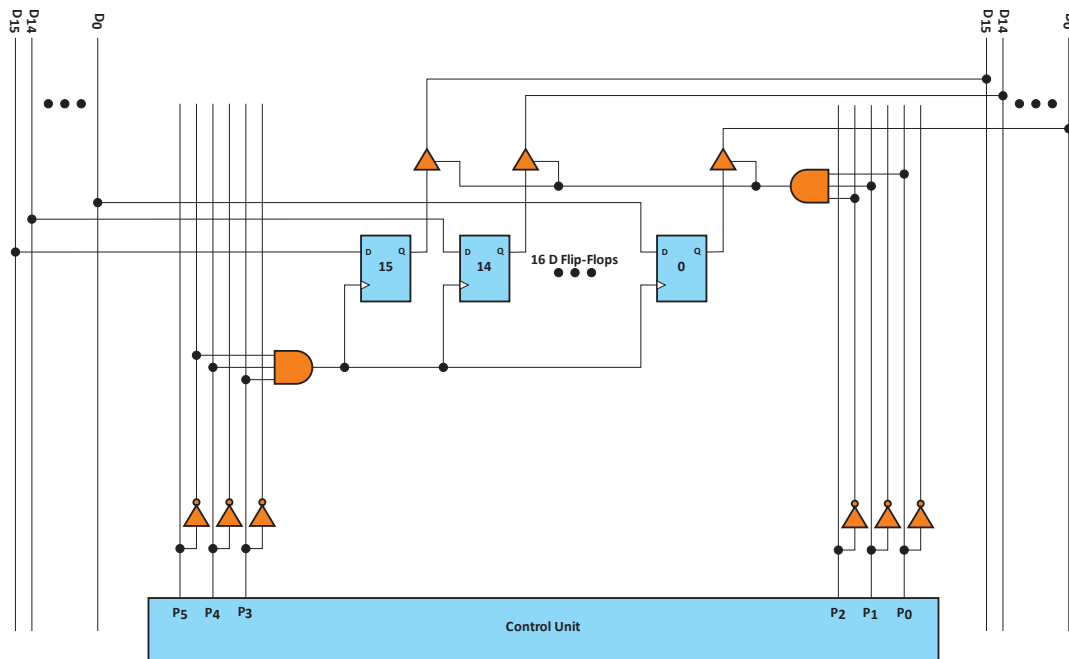
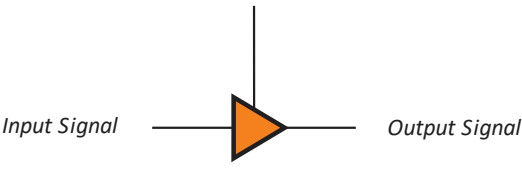
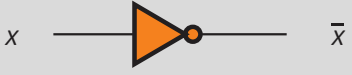


Figure 4.15 Connection of MARIE's MBR to the Datapath

Device	Operation
<p>Switch 0=Off 1=On</p> 	<p>Tri-state device:</p> <ul style="list-style-type: none"> If the switch is off, then the input signal is NOT transmitted to the output signal. If the switch is on, then the input signal IS transmitted to the output signal.
	<p>Inverter:</p> <ul style="list-style-type: none"> If $x = 0$, then $\bar{x} = 1$ If $x = 1$, then $\bar{x} = 0$

- The set of signals $\{P_2, P_1, P_0\}$ are assigned to **read** values put on the data bus.
- The set of signals $\{P_5, P_4, P_3\}$ are assigned to **write** values to the data bus.
- Please note that a signal has a default value of 0. The significance of this feature is that to make the hypothetical transfer $IR \leftarrow MAR$, we need only assign $[P_5, P_4, P_3] \leftarrow 111$ (7) and $[P_2, P_1, P_0] \leftarrow 001$ (1). However, in practice, we only assign $P_0 \leftarrow 1$, because the other signals P_2 and P_1 are, by default, zero (0).
- We can imagine sets of D-Flip-Flops for the other registers MAR, PC, AC, InREG, and OutReg.

Bus Address	Device
0	Main Memory
1	MAR
2	PC
3	MBR
4	AC
5	InReg
6	OutReg
7	IR

MARIE's Datapath Addresses

ALU Control Signals		ALU Response
A_1	A_0	
0	0	Do Nothing
0	1	$AC \leftarrow AC + MBR$
1	0	$AC \leftarrow AC - MBR$
1	1	$AC \leftarrow 0$ (Clear)

Table 4.8 ALU Control Signals and Response

L_{ALT}	Action
0	Load the AC from the Data bus Load the MBR from the Data bus
1	Load the AC from the ALU Load the MBR from the AC

M_R	M_W	Action
0	0	Do Nothing
0	1	Memory Write Enable
1	0	Memory Read Enable
1	1	(Impossible)

I_{PC}	Action
0	Do Nothing
1	$PC \leftarrow PC + 1$

T_0	Q_0	T_1	Q_1	T_2	Q_2	T_3	Q_3	T_4
1	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
0	0	0	1	1	0	0	0	0
0	0	0	0	0	1	1	0	0
0	0	0	0	0	0	0	1	1
1	0	0	0	0	0	0	0	0

- Text asserts seven clock cycles, $T_0 - T_6$, are needed. Find the longest instruction, JnS .

- Including the clock cycles needed to fetch an instruction, ten clock cycles are needed, $T_0 - T_9$.

Add X		
Control Signals	RTN	Comment
$T_0P_3P_1$	$MAR \leftarrow PC$	Fetch
$T_1P_5P_4P_3M_R$	$IR \leftarrow M[MAR]$	
T_2I_{PC}	$PC \leftarrow PC + 1$	
$T_3P_3P_2P_1P_0$	$MAR \leftarrow X(IR[11 - 0])$	Decode
$T_4P_4P_3M_R$	$MBR \leftarrow M[MAR]$	Execute
$T_5P_5A_0L_{ALT}C_R$	$AC \leftarrow AC + MBR$	

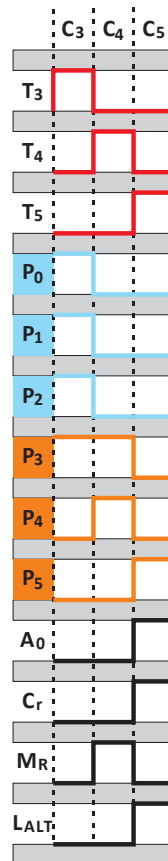


Figure 4.16 Timing Diagram for the Microoperations of MARIE's Add Instruction

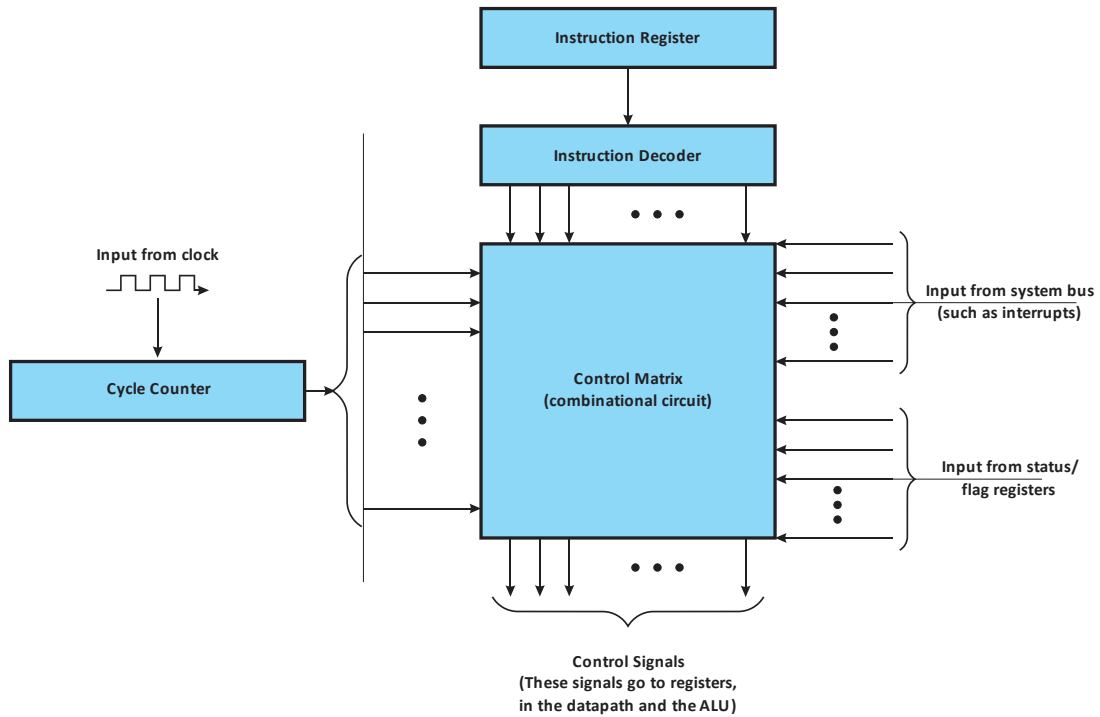


Figure 4.17 Hardwired Control Loop

Figure 4.18 Partial Instruction Decoder for MARIE's Instruction Set

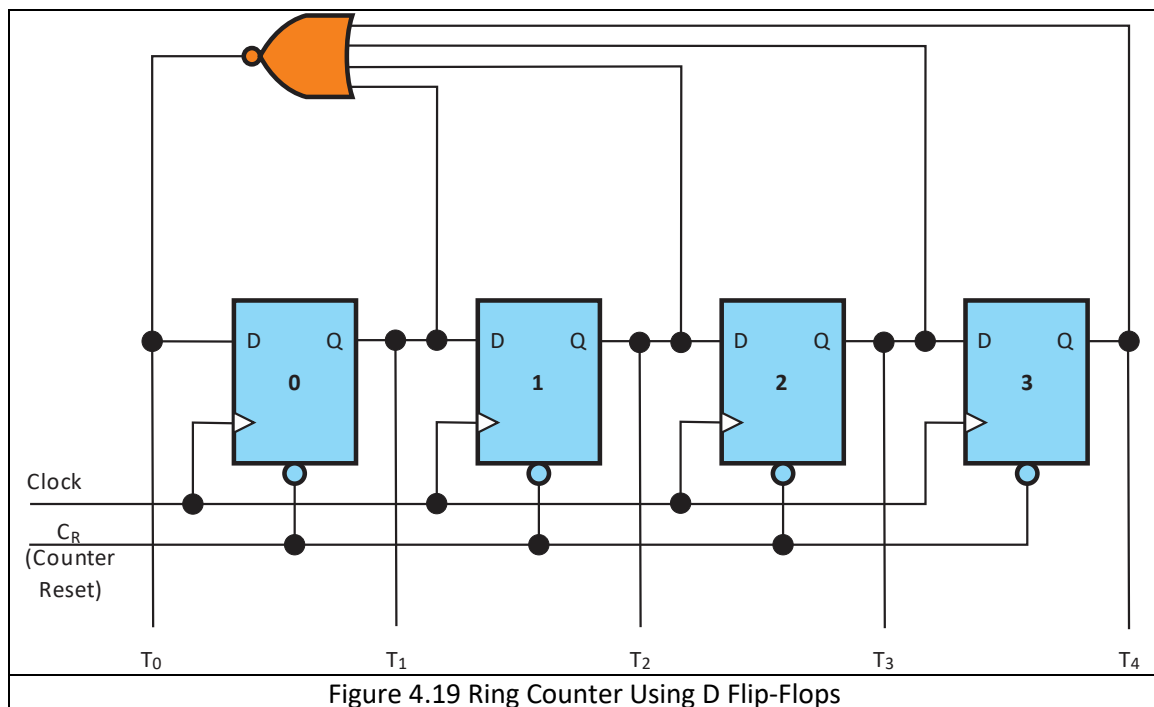


Figure 4.19 Ring Counter Using D Flip-Flops

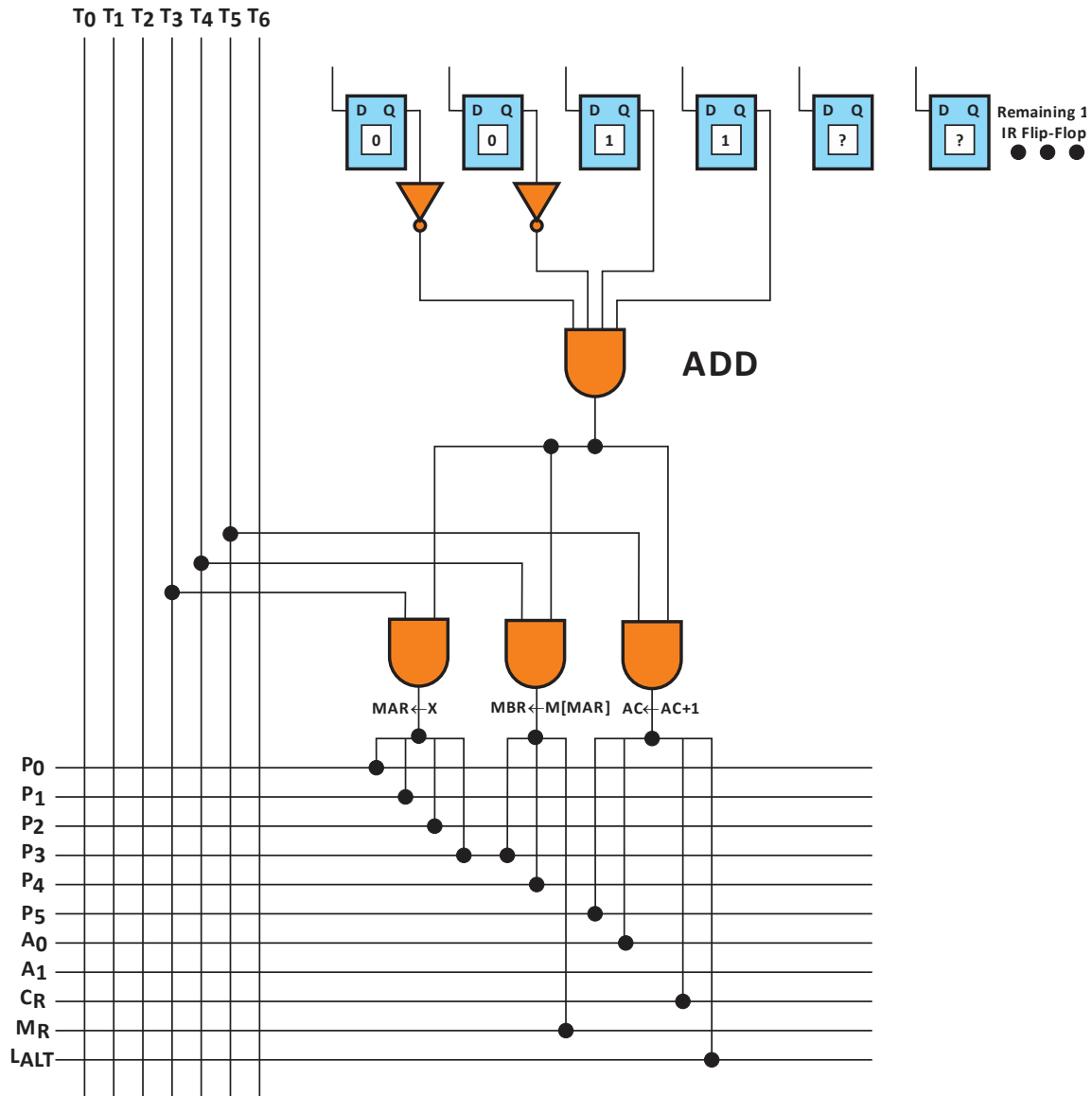


Figure 4.20 Combinational Logic for Signal Controls of MARIE's Add Instruction

4.13.3 Microprogrammed Control

- In microprogrammed control, instruction **microcode** produces the necessary control signals.

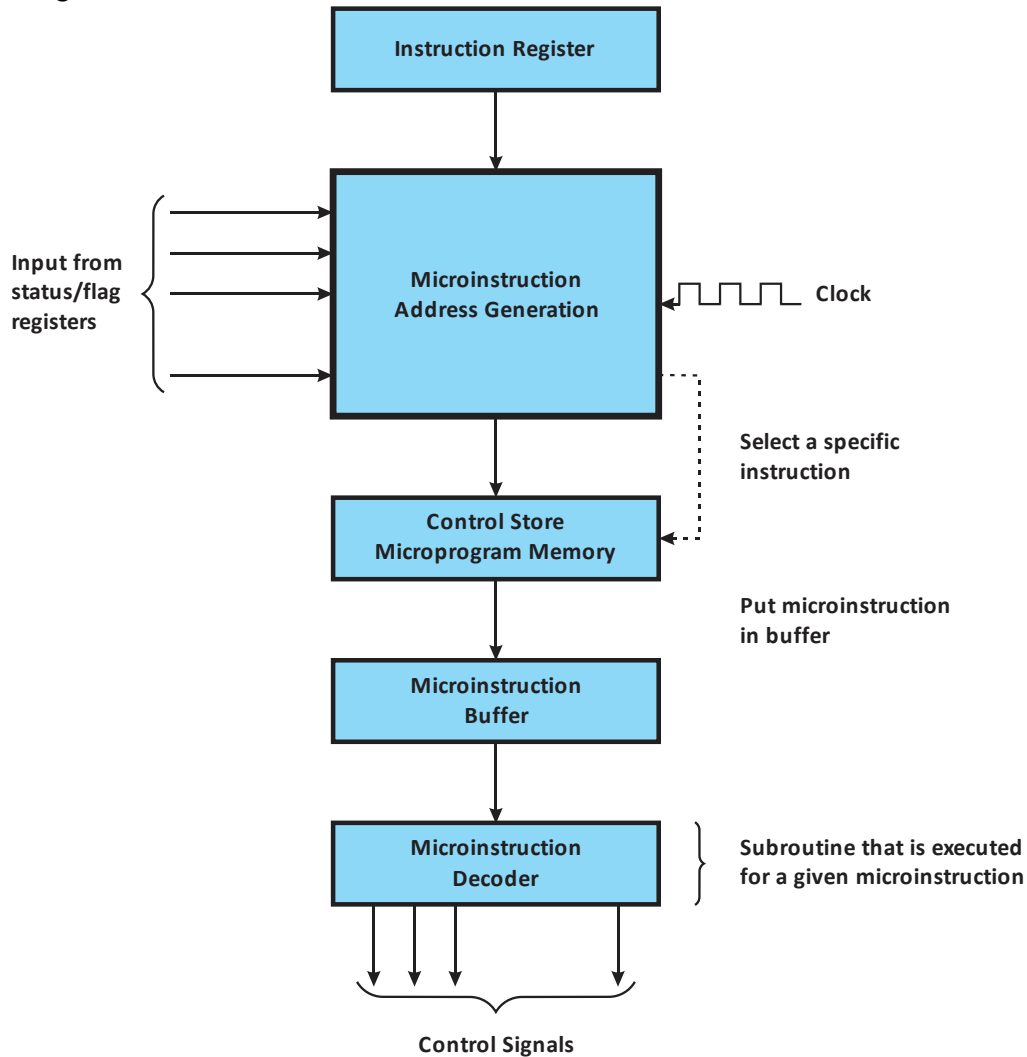


Figure 4.21 Microprogrammed Control Unit

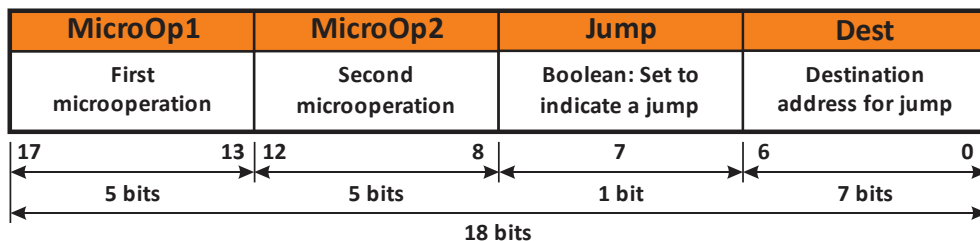


Figure 4.22 MARIE's Microinstruction Format

- All machine instructions are input into a special program, the **microprogram**, that converts machine instructions of 0s and 1s into control signals.

- The microprogram is, essentially, an interpreter, written in microcode, that is stored in **firmware** (ROM, PROM, or EPROM), which is often referred to as the control store.
- The **microsequencer** is like the program counter that selects the next microinstruction to execute.
- MicroOp1 and MicroOp2 are binary codes for each unique microoperation specified in the RTN for MARIE's instruction set.
- So far, we have defined 22 unique microoperations.
- We need a NOP – no operation microcode.
- We need a comparison microoperation that compares the bit pattern in the first 4 bits of the instruction register (IR[14-12]) to a literal value that is in the first 4 bits of the MicoOp2 field.
- MARIE's entire microprogram consists of fewer than 128 statements, so each statement can be uniquely identified by seven (7) bits. Each microinstruction has a seven-bit address.

MicroOp Code	Microoperation	MicoOp Code	Microoperation
00000	NOP	01101	MBR \leftarrow M[MAR]
00001	AC \leftarrow 0	01110	OutREG \leftarrow AC
00010	AC \leftarrow MBR	01111	PC \leftarrow IR[11 - 0]
00011	AC \leftarrow AC - MBR	10000	PC \leftarrow MBR
00100	AC \leftarrow AC + MBR	10001	PC \leftarrow PC + 1
00101	AC \leftarrow InREG	10010	If AC = 0
00110	IR \leftarrow M[MAR]	10011	If AC > 0
00111	M[MAR] \leftarrow MBR	10100	If AC < 0
01000	MAR \leftarrow IR[11 - 0]	10101	If IR[11 - 10] = 00
01001	MAR \leftarrow MBR	10110	If IR[11 - 10] = 01
01010	MAR \leftarrow PC	10111	If IR[11 - 10] = 10
01011	MAR \leftarrow X	11000	If IR[15 - 12] = MicroOp2[4 - 1]
01100	MBR \leftarrow AC		

Table 4.9 Microoperation Codes and Corresponding MARIE RTL

Address	MicroOp1	MicroOp2	Jump	Dest
000 0000	MAR \leftarrow PC	NOP	0	000 0000
000 0001	IR \leftarrow M[MAR]	NOP	0	000 0000
000 0010	PC \leftarrow PC + 1	NOP	0	000 0000
000 0011	MAR \leftarrow IR[11 - 0]	NOP	0	000 0000
000 0100	If IR[15 - 12] = MicroOp2[4 - 1]	00000 JnS X	1	010 000
000 0101	If IR[15 - 12] = MicroOp2[4 - 1]	00010 Load X	1	010 0111
000 0110	If IR[15 - 12] = MicroOp2[4 - 1]	00100 Store X	1	010 1010
000 0111	If IR[15 - 12] = MicroOp2[4 - 1]	00110 Add X	1	010 1100
000 1000	If IR[15 - 12] = MicroOp2[4 - 1]	01000 Subt X	1	010 1111
...
...
010 1010	MAR \leftarrow X	MBR \leftarrow AC	0	000 0000
010 1011	M[MAR] \leftarrow MBR	NOP	1	000 0000
010 1100	MAR \leftarrow X	NOP	0	000 0000
010 1101	M[MAR] \leftarrow MBR	NOP	0	000 0000
010 1110	AC \leftarrow AC + MBR	NOP	1	000 0000
010 1111	MAR \leftarrow X	NOP	0	000 0000
011 0000	M[MAR] \leftarrow MBR	NOP	0	000 0000
011 0001	AC \leftarrow AC - MBR	NOP	1	000 0000
...

FIGURE 4.23 Selected Statements in MARIE's Microprogram

- It's important to remember that a microprogrammed control unit works like a system-in-miniature.
- Microinstructions are fetched, decoded, and executed in the same manner as regular instructions.
- This extra level of instruction interpretation is what makes microprogrammed control slower than hardwired control.
- The advantages of microprogrammed control are that it can support very complicated instructions and only the microprogram needs to be changed if the instruction set changes (or an error is found).